

## SECOND ORDER DEVICES

### CAPACITOR

A DEVICE WHICH STORES ENERGY IN AN ELECTRIC FIELD. COMPRISED OF TWO CONDUCTIVE "PLATES" SEPARATED BY A DIELECTRIC MEDIUM. CHARGE STORED ON THE PLATES IS EQUAL TO THE PRODUCT OF THE VOLTAGE ACROSS THE PLATES AND THE CAPACITANCE OF THE DEVICE.

$$q = C v_c \rightarrow \frac{dq}{dt} = \frac{d}{dt}(C v_c) \rightarrow i_c = C \frac{dv_c}{dt}$$

$$\frac{dv_c}{dt} = C^{-1} i_c \rightarrow \int \frac{dv_c}{dt} dt = \int C^{-1} i_c dt \rightarrow v_c = C^{-1} \int i_c dt$$

REACTANCE IS FREQUENCY DEPENDANT AND OF THE FORM

$$X_c = \frac{1}{2\pi f C} = \frac{1}{\omega C}$$

WE CAN ALSO INVESTIGATE THE COMPLEX IMPEDANCE IN THE LAPLACE DOMAIN BY STARTING WITH ONE OF OUR  $v_c$  OR  $i_c$  EQUATIONS IN THE TIME DOMAIN:

$$v_c(t) = \frac{1}{C} \int i_c dt$$

$$\mathcal{L}\{v_c(t)\} = \mathcal{L}\left\{\frac{1}{C} \int i_c dt\right\}$$

$$V_c(s) = \frac{1}{C} \mathcal{L}\left\{\int i_c dt\right\}$$

$$V_c(s) = \frac{1}{C} \times \frac{1}{s} \times I_c(s)$$

$$\frac{V_c(s)}{I_c(s)} = \frac{1}{sC}$$

$$Z_c(s) = \frac{1}{sC}$$